

# PHYS 3142 Spring 2019

## Computational Methods in Physics


### Assignment 3

**Due: 18 Mar 2019**

Before you submit your assignment, do remember:

1. the due day
2. submit a report which contains your figures and results along with your code
3. make sure your code can run
4. do not upload a compressed file(e.g. rar, zip, . . . )

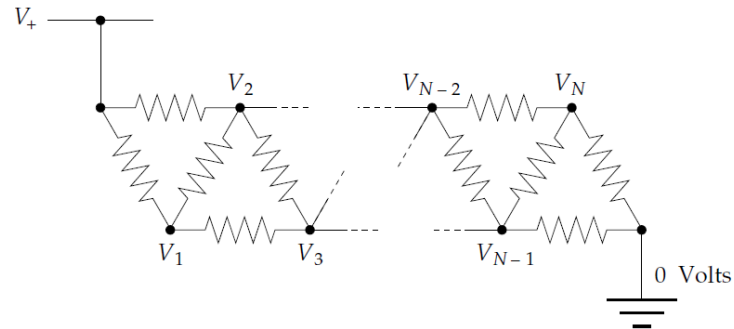1. Consider a long chain of resistors wired up like this:  
All the resistors have the same resistance  $R$ . The power rail at the top is at voltage  $V_+ = 5V$ .  
The problem is to find the voltages  $V_1 \dots V_N$  at the internal points in the circuit.



- (a) Using Ohm's law and the Kirchhoff current law, which says that the total net current flow out of (or into) any junction in a circuit must be zero, show that when  $N = 3$ , the voltages  $V_1, V_2, V_3$  satisfy the equations

$$3V_1 - V_2 - V_3 = V_+$$

$$4V_2 - V_1 - V_3 = V_+$$

$$3V_3 - V_1 - V_2 = 0$$

Express these equations in vector form  $A\mathbf{v} = \mathbf{w}$  and find the values of the matrix  $A$  and the vector  $\mathbf{w}$ . Factorize the matrix  $A$  analytically using the LU decomposition. Then solve the simultaneous equations by either using the Gaussian elimination or LU decomposition. Also write a simple program and use `numpy.linalg` to check your result.

(Answer:  $V_1=3.125V, V_2=2.5V, V_3=1.875V$ )

- (b) If there are  $N$  internal junctions, show that the voltages  $V_1 \dots V_N$  satisfy the equations:

$$3V_1 - V_2 - V_3 = V_+,$$

$$-V_1 + 4V_2 - V_3 - V_4 = V_+,$$

$$-V_1 - V_2 + 4V_3 - V_4 - V_5 = 0,$$

...

$$-V_{i-2} - V_{i-1} + 4V_i - V_{i+1} - V_{i+2} = 0,$$

...

$$-V_{N-3} - V_{N-2} + 4V_{N-1} - V_N = 0,$$

$$-V_{N-2} - V_{N-1} + 3V_N = 0.$$

Express these equations in vector form  $\mathbf{A}\mathbf{v} = \mathbf{w}$  and find the values of the matrix  $\mathbf{A}$  and the vector  $\mathbf{w}$ .

- (c) Write a program to use `solve` in `numpy.linalg` to solve for the values of the  $V_i$  when there are  $N = 6$  internal junctions with unknown voltages. (Hint: All the values of  $V_i$  should lie between zero and 5V. If they don't, something is wrong.)  
(Answer:  $V_1 = 3.7254902$  V,  $V_2 = 3.43137255$  V,  $V_3 = 2.74509804$  V,  $V_4 = 2.25490196$  V,  $V_5 = 1.56862745$  V,  $V_6 = 1.2745098$  V)

- (d) Now repeat your calculation for the case where there are  $N = 10\,000$  internal junctions.

This part is not possible using standard tools like the `solve` function. You need to make use of the fact that the matrix  $\mathbf{A}$  is banded and use the banded function from the file `banded.py`, which can be downloaded from the link:

<http://www-personal.umich.edu/~mejn/cp/programs/banded.py>

*Hint: By writing the matrix for  $N=6$ , you can easily see that on each non-vanishing (sub-)diagonal, most of the elements are identical. And you should use this fact to construct the rectangular matrix used in `banded.py`. Please also refer to the lecture note (`linear algebra.pdf`) we have discussed in the class.*

(Answer:  $V_1 = 4.99888\dots$  V,  $V_2 = 4.99861\dots$  V,  $V_3 = 4.99802\dots$  V ...,  $V_{9998} = 0.00197\dots$  V,  $V_{9999} = 0.00138\dots$  V,  $V_{10000} = 0.00111\dots$  V)